
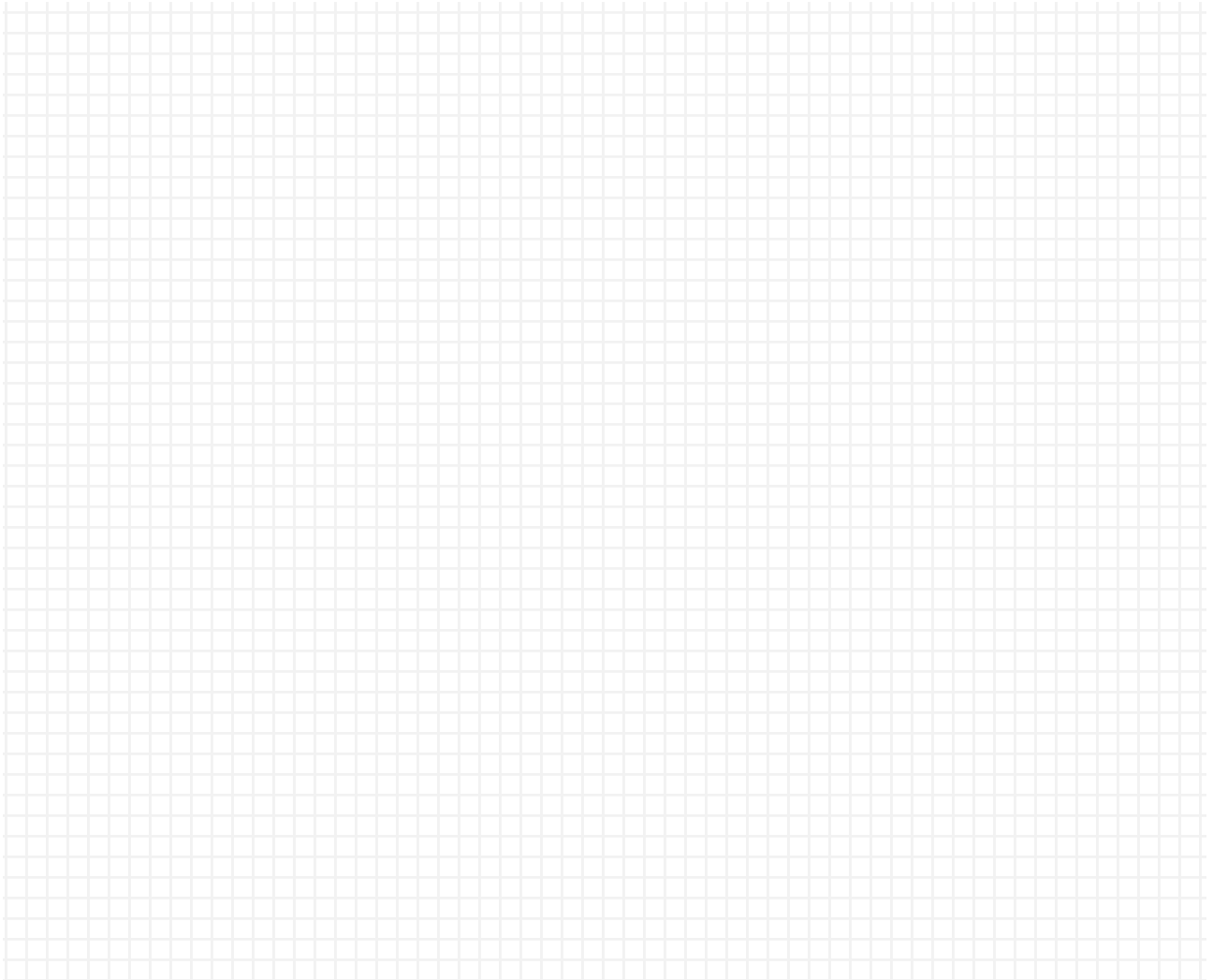


CHAPTER 2

NOISE IN BIOMEDICAL INSTRUMENTATION

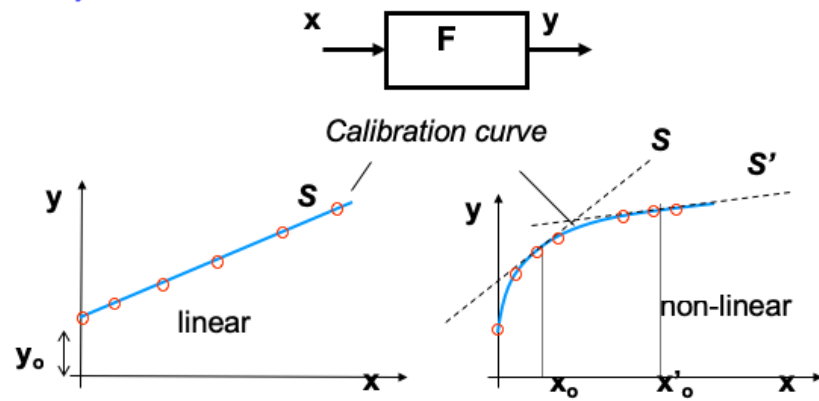

Static characteristics of a measurement system (reminder)



■ Offset


$$y = S \cdot x + y_o$$

■ Sensitivity


$$S = \left(\frac{\Delta y}{\Delta x} \right)_{x=x_o}$$

Static characteristics (reminder)


■ Linearity

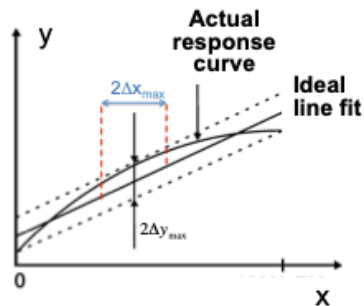

■ Repeatability

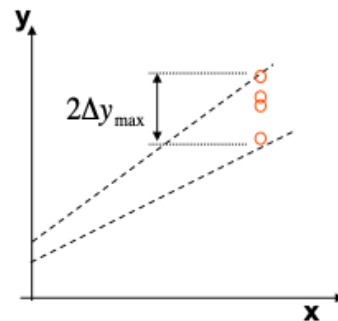

■ Hysteresis

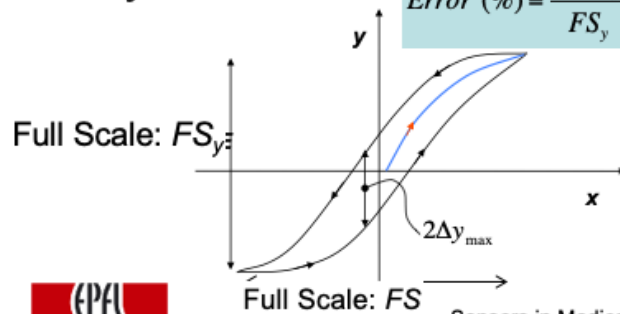

$$\text{Error (\%)} = \frac{\pm \Delta y_{\max}}{FS_y} = \frac{\pm \Delta x_{\max}}{FS}$$

■ Stability: conserving same output when input is constant over time

■ Drift: low change over time

Example: error calculation of a pressure sensor

Pressure range	FS	0-200	kPa
Offset	V _{off}	±1	mV
Sensitivity	ΔV/ΔP	0.2	mV/kPa
Linearity		±0.5%	FS
Hysteresis		±0.5%	FS
Temperature effect on FS (0 to 50°C, T _{ref} =25°C)	T _{FS}	±2%	FS
Temperature effect on Offset (0 to 50°C, T _{ref} =25°C)	T _{OFF}	±1	mV
Offset Stability		±0.5%	FS

$$Error_{max} = \pm \sum_i |\Delta x_i|$$


$$Error_{probable} = \pm \sqrt{\Delta x_i^2}$$

Error_{OFF}=±5kPa, Error_{lin}=±1kPa, Error_{Hyst}=±1kPa
 Error_{T_{FS}}=±4kPa, Error_{T_{OFF}}=±5kPa, Error_{Stab}=±1kPa
 Error maximum=±(5+1+1+4+5+1)=±17kPa
 Error probable=±√(5²+1²+1²+4²+5²+1²)=±8.3kPa



ÉCOLE POLYTECHNIQUE
FÉDÉRALE DE LAUSANNE

Dynamic transfer characteristics

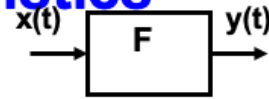

■ Ordinary Differential Equations

$$a_n \frac{d^n y}{dt^n} + a_{n-1} \frac{d^{n-1} y}{dt^{n-1}} + \dots + a_1 \frac{dy}{dt} + a_0 y = x(t) \quad (1)$$

■ Zero order

■ e.g.: goniometer

$$y = S \cdot x \quad S: \text{sensitivity}$$

■ 1st order

■ e.g.: temperature sensor

$$\tau \frac{dy}{dt} + y = S \cdot x \quad \tau: \text{time constant}$$

■ 2nd order

■ e.g.: accelerometer

$$\frac{1}{\omega_o^2} \frac{d^2 y}{dt^2} + \frac{2\xi}{\omega_o} \frac{dy}{dt} + y = S \cdot x$$

ω_o : resonant angular velocity

ξ : damping coefficient




D'une manière générale, la variation en fonction du temps des valeurs de la grandeur d'entrée x génère des variations des valeurs de la grandeur de sortie. On peut modéliser cette correspondance par l'équation différentielle (1) où n désigne l'ordre du système de mesure dynamique. En général, on limite la modélisation aux systèmes d'ordre 0, 1 et 2.

Les coefficients a_n sont déterminés théoriquement par modélisation, ou expérimentalement par l'analyse du comportement du système soumis à des sollicitations appropriées. Ces sollicitations sont les formes typiques du signal x : impulsion, saut unitaire, sinusoïdal.


General model

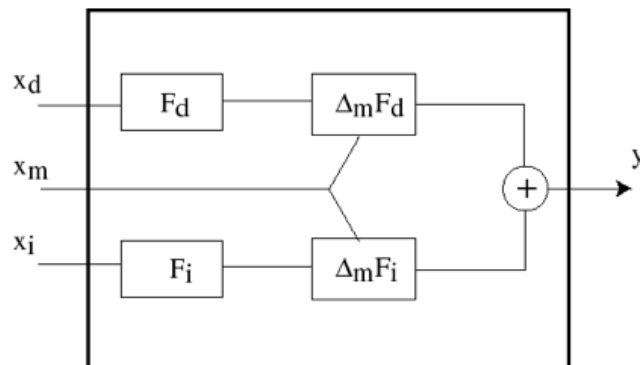- x_d : desired value, measurand, with transfer function F_d
- x_m : modifying value
- x_i : interfering value, with transfer function F_i



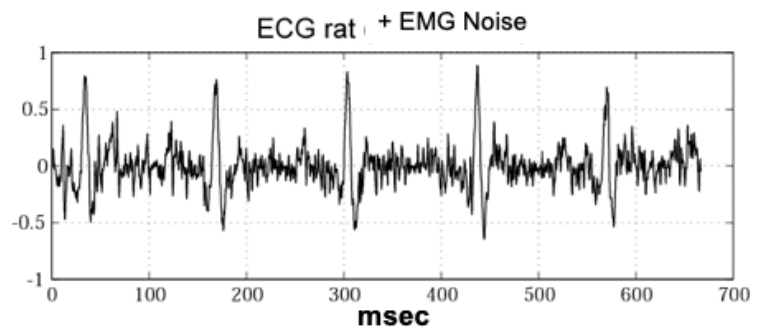
Examples (M: modifying, I: Interfering)

- Power line interference, 50Hz, white noise **I**
- Electrode movement **M**
- Signals emanating from other devices nearby: **I**
electrosurgery
- EMG noise when measuring the ECG. **I**



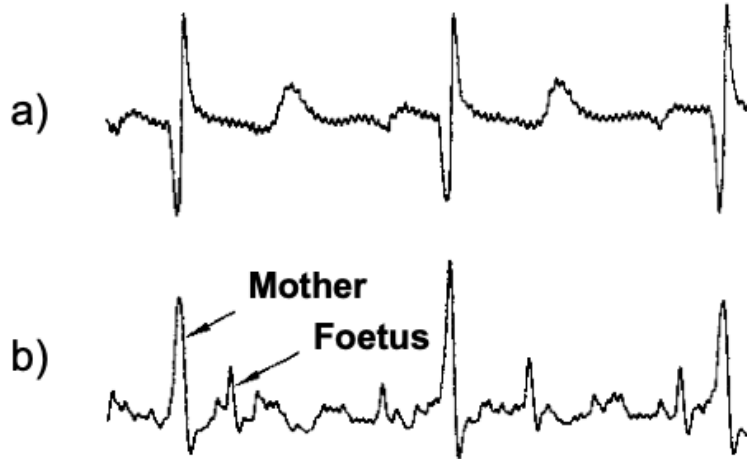Examples of interfering value

- The heart rate of the mother can overshadow that of the foetus



Noise characteristics

- Amplitude

- Ratio of signal to noise

Signal to Noise Ratio: **SNR**


$$SNR = \frac{s}{n} = \frac{(\text{desired value}, V)^2}{(\text{deviating value}, V)^2} = \frac{\text{Signal Power}}{\text{Noise Power}}$$

- While performing a measurement, we aim to obtain a high SNR by increasing the signal amplitude and decreasing the noise amplitude.
- The SNR is expressed in dB.

$$SNR_{dB} = 10 \log \frac{s}{n}$$

Noise characteristics

- Bandwidth of noise B_N

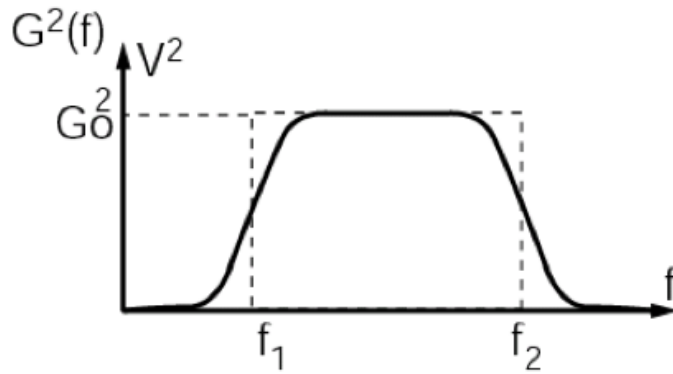

$$B_N = \frac{1}{G_o^2} \int_0^{\infty} G^2(f) df$$

Miscellaneous types of intrinsic noise

- **Thermal noise (Johnson)**

In a conductor: the random movements of the atoms are transmitted to the conducting electrons

- **Shot noise**

Random fluctuation of current associated with crossing an electric potential barrier

- **1/f noise**

Instability and drift phenomena, non-homogeneities of materials, contacts between conductors

Intrinsic noise source

- Thermal noise


In a conductor: the random movements of the atoms are transmitted to the conducting electrons

$$U_{Neff}^2 = 4KTR_N B_N$$

U_{Neff}^2 : noise strength

T : conductor temperature in ° K

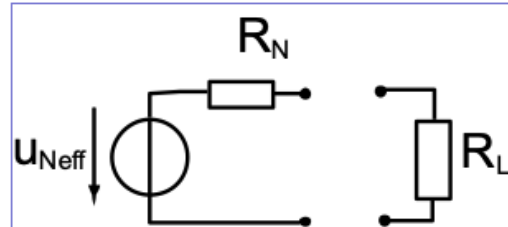K : Boltzmann constant = 1.38×10^{-23} J/K



$$U_{Neff} / \sqrt{B_N} = 0.13 \sqrt{R_N} \text{ (}\eta\text{V}/\sqrt{\text{Hz}} \text{)} \quad (20^\circ\text{C})$$

Spectral density of noise

- The **psd**: **p**ower **s**pectral **d**ensity, Φ_N is the energy of the noise produced by a conductor at each cycle

$$\phi_N = \frac{P_N}{B_N}$$

W/Hz (joule/cycle)

Example: amplifier INA118 (BB)

Parameter	Conditions	Type INA118PB	Units
Input noise voltage	G = 1000		
f = 10 Hz		11	nV/\sqrt{Hz}
f = 100 Hz		10	nV/\sqrt{Hz}
f = 1000 Hz		10	nV/\sqrt{Hz}
$f_B = 0.1 \text{ Hz to } 10 \text{ Hz}$		0.28	$\mu Vp - p$
Noise current			
f = 10 Hz		2.0	pA/\sqrt{Hz}
f = 1000 Hz		0.3	pA/\sqrt{Hz}
$f_B = 0.1 \text{ Hz to } 10 \text{ Hz}$		80	$pAp - p$


- Example: for a bandwidth of 1kHz, the input noise is

$$10 \cdot 10^{-9} \cdot \sqrt{1000} = 0.32 \mu V.$$

Shot noise or Schottky noise

- White noise, normal distribution
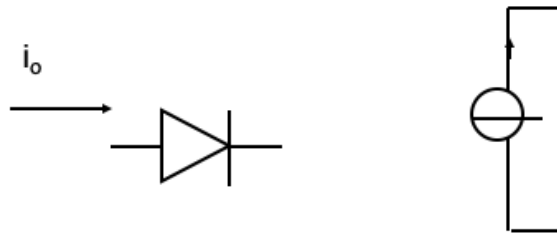
$$I_{b,eff} = \sqrt{2ei_oB_N} \quad e=1.6 \times 10^{-19}C$$



Additional 1/f noise

- $\phi_N = \frac{\lambda}{f}$

λ = constant depending on current amplitude

- Power of noise generated in the frequency bandwidth of $B_N = [f_1, f_2]$

$$P_N = \int_{f_1}^{f_2} \frac{\lambda}{f} df = \lambda \ln \frac{f_2}{f_1}$$

Extrinsic noise sources

- Interferences

- 50 Hz from electrical power lines.



- Devices

- Electrosurgery 500 kHz – 3 MHz
 - Diathermy 500 kHz – 3000 MHz

Very high frequencies compared to those of physiological signals, but ...

Noise source: interferences

- At the input level of measurement devices, the interferences can be rectified and thus demodulated for erroneous DC (offset) components
- Noise is mainly decreased by **shielding**


Artefact

- EMG while measuring the ECG




- Electrode movement : change in electrode-skin contact impedance (flexible cables, gel)
- Skin movement
- Mechanical movement : vibrations
- Voltage drift


Example (see exercise)

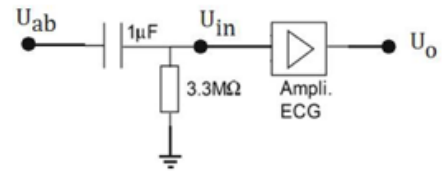

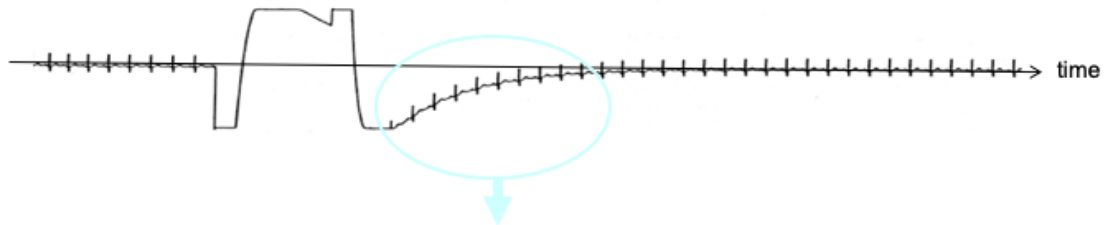
- Effect of a transition voltage (depend on RC value)



Noise due to capacitive coupling

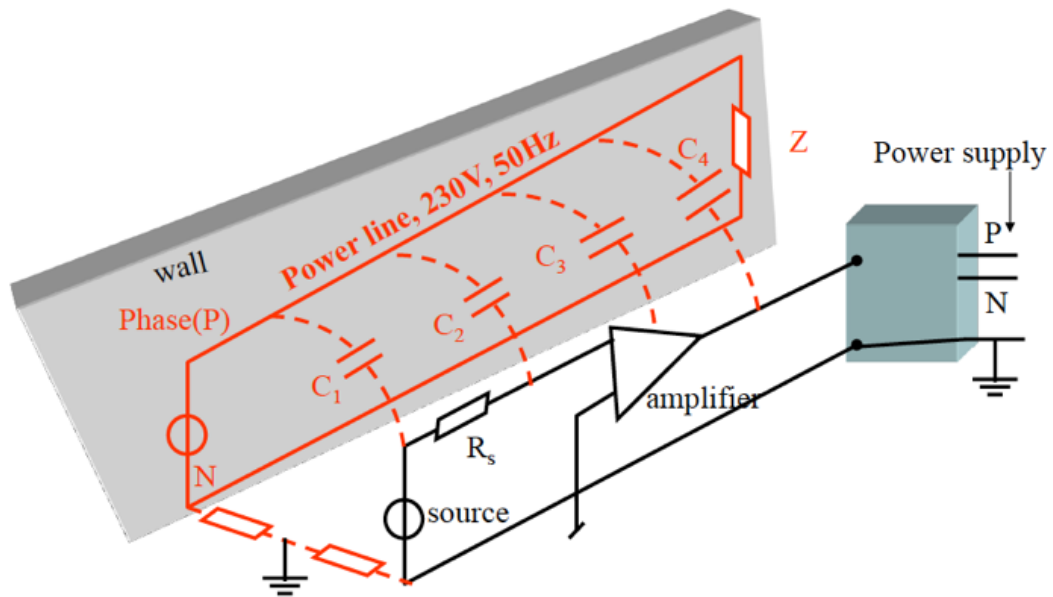

Coupling with wires and devices

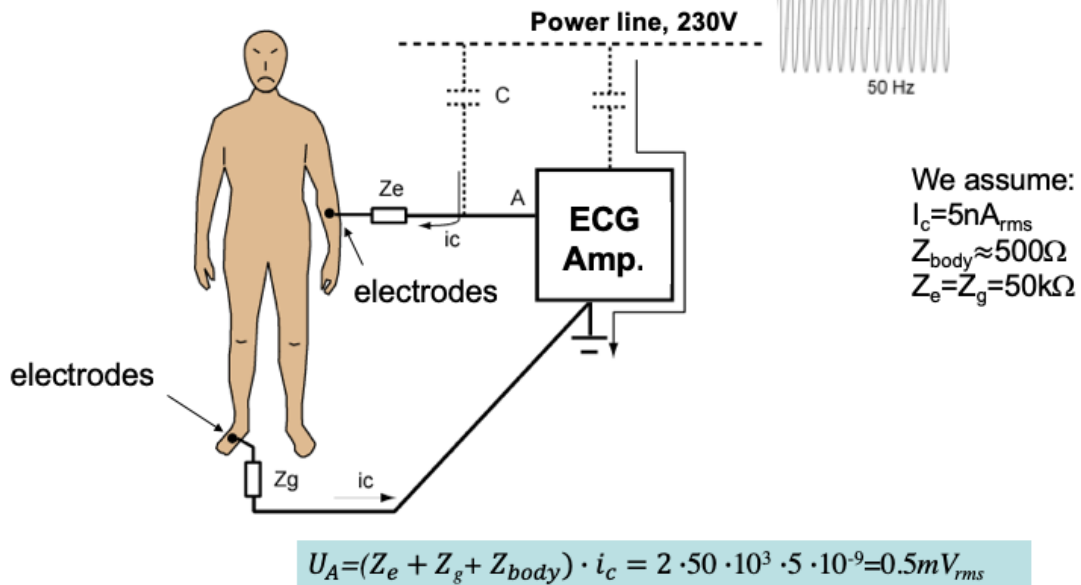

Coupling with the subject

$$U_{mc} = Z_g \cdot i_c$$


For $Z_g = 50k\Omega$ and $i_c = 0.2\mu A_{rms}$,

$$U_{mc} = 50 \cdot 10^3 \cdot 0.2 \cdot 10^{-6} = 10mV_{rms}$$


Noise at the input of the amplifier:

($Z_{in} = 10M\Omega$, $Z_e = 50k\Omega$)

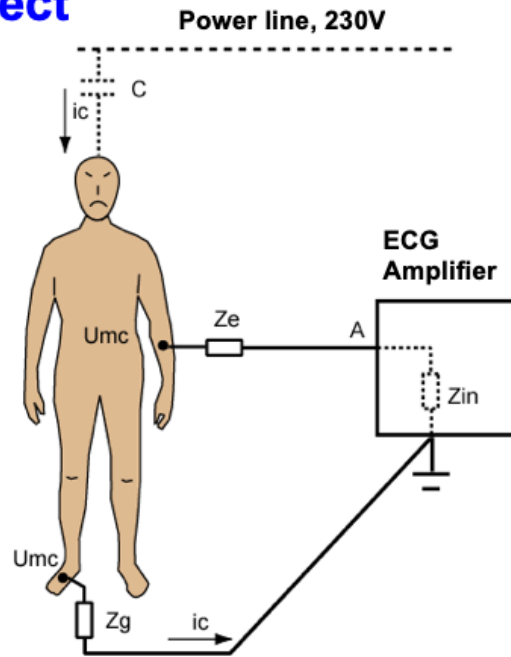
$$U_A = \frac{Z_{in}}{Z_{in} + Z_e} U_{mc} \cong 10mV_{rms}!!$$



Magnetic fields

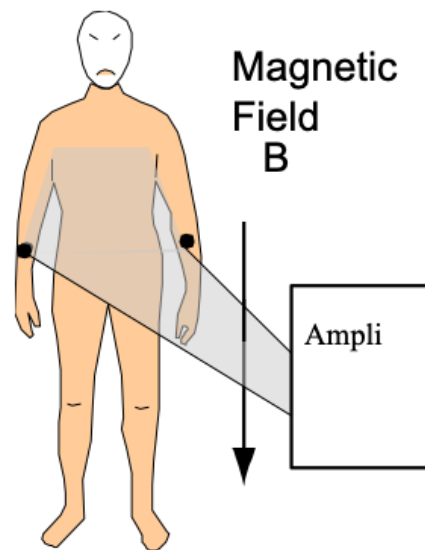

Magnetic coupling

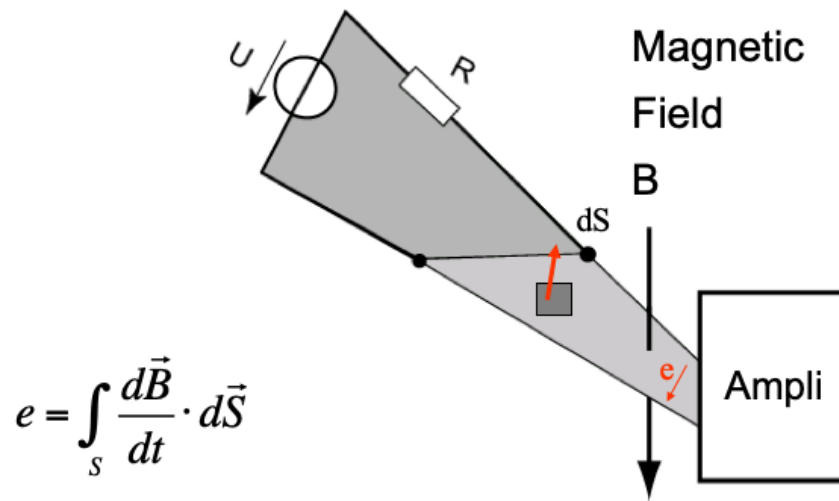

Decreasing noise: coupling with wires

- Differential amplifier

$$U_{AB} = U_A - U_B = Z_e \cdot i_{c2} - Z'_e \cdot i_{c1}$$

If the two wires are close :


$$i_{c1} = i_{c2} = i_c$$

$$U_{AB} = U_A - U_B = (Z_e - Z'_e) \cdot i_c$$

for $Z_e - Z'_e = 25k\Omega$ and $i_c = 5nA_{rms}$

$$U_{AB} = 125\mu V_{rms}$$

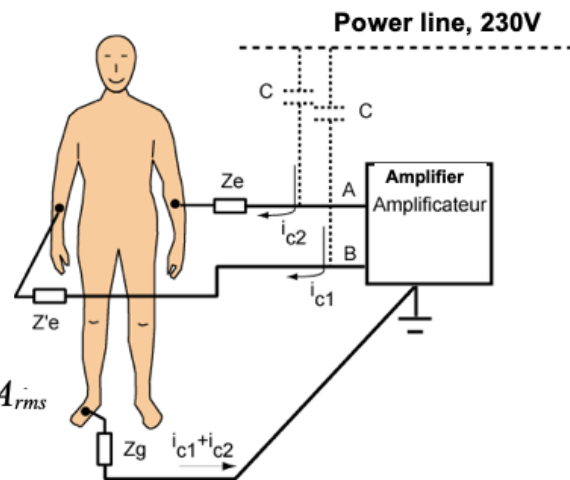Without differential amplifier : $U_{AB} = 0.5mV_{rms}$



Decreasing noise : coupling with the subject

- Common mode voltage of the **source**


$$U_{mc} = i_c \cdot Z_g$$

$$\text{For } Z_g = 50k\Omega$$

$$\text{and } i_c = 0.2\mu A_{rms}$$

$$U_{mc} = 10mV_{rms}$$

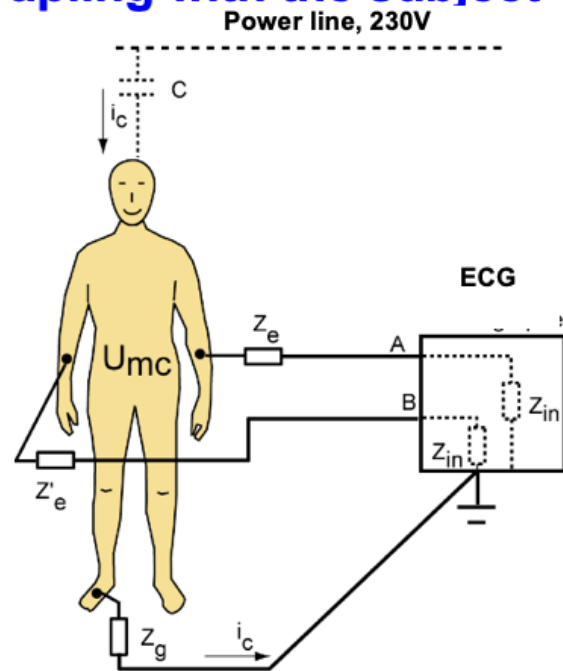Higher in amplitude than
ECG voltage to measure!



$I_c = 0.2 \text{ mA}$?

Example

- For $Z_{in} \gg Z_e$ and $Z_{in} \gg Z'_e$ ($U_d = 0$):



$$U_{AB} = U_A - U_B$$

$$= U_{mc} \left(\frac{Z_{in}}{Z_{in} + Z_e} - \frac{Z_{in}}{Z_{in} + Z'_e} \right)$$

$$= \frac{Z'_e - Z_e}{Z_{in}} U_{mc}$$

$$U_{AB} = 10mV \cdot \frac{20k\Omega}{5M\Omega} = 40\mu V_{rms}$$

Power line, 230V

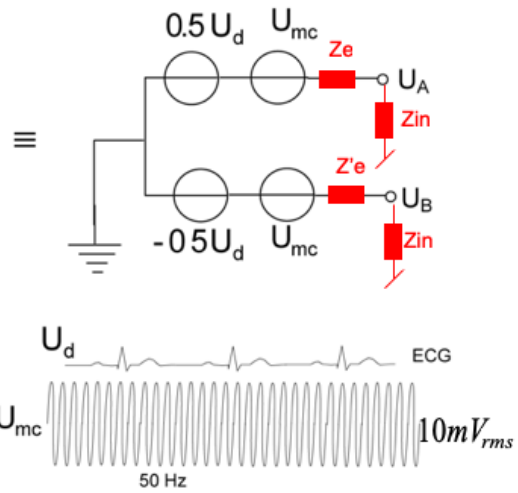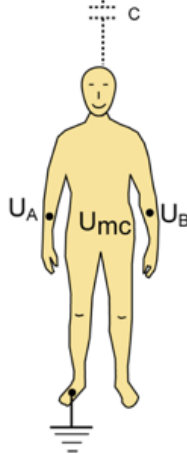

Common mode voltage : definition

U_{mc}


- U_{mc} : Voltage common to U_A and U_B , does not provide any information

$$U_{mc} = \frac{U_A + U_B}{2}$$

$$U_{AB} = U_A - U_B$$

$$U_A = U_{mc} + \frac{U_{AB}}{2}$$

$$U_B = U_{mc} - \frac{U_{AB}}{2}$$

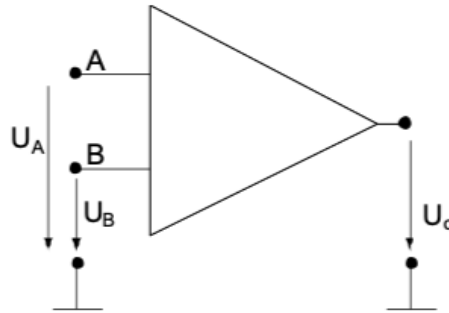

Common mode voltage : origins

- Common mode voltage due to power source


$$U_B = \frac{U}{2}$$

$$U_A = \frac{U}{2} + U_{AB} = \frac{U}{2} + \frac{\Delta R}{4R} U$$

$$U_{mc} \cong \frac{U}{2}$$

- For $U = 20V$ and $\frac{\Delta R}{R} = 0.01$:


$$U_{mc} = 10V, \quad U_{AB} = 0.05V$$

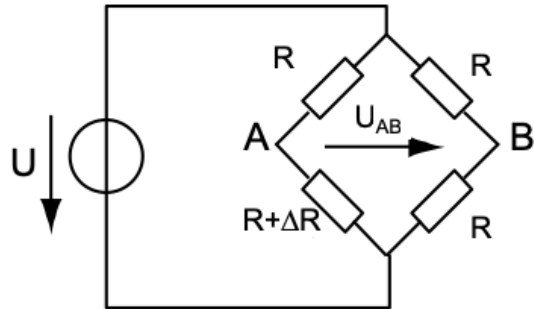

U_{mc} can be many times higher than U_{AB}

Common mode voltage : origins

- Common mode voltage due to **ground**

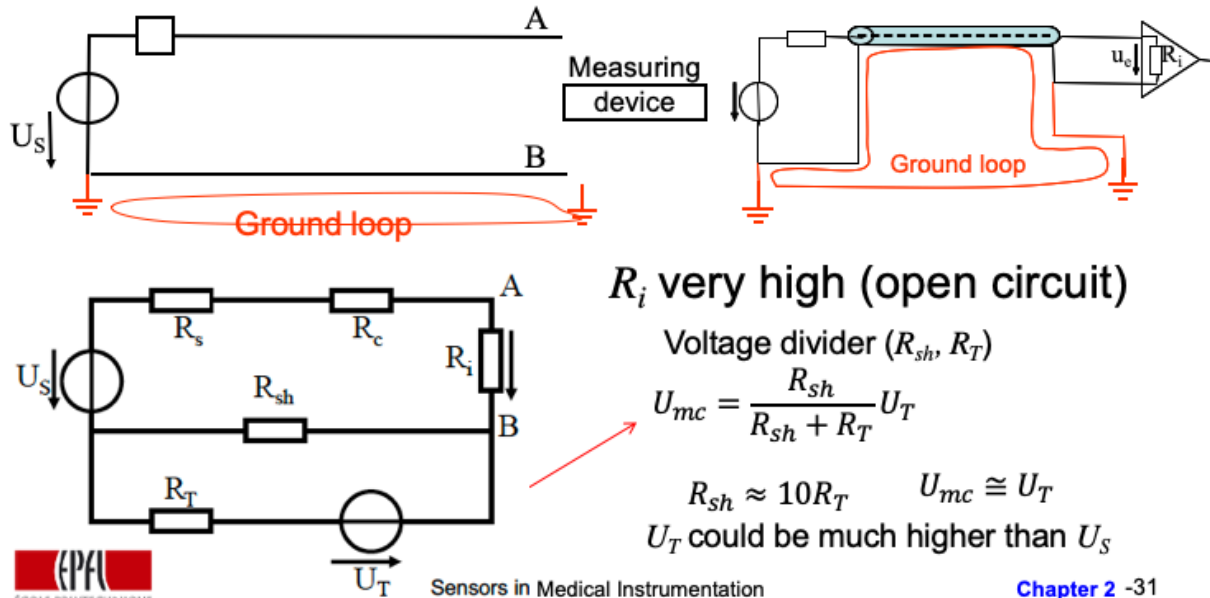

Common mode voltage : origins

- Common mode voltage of the **source**


$$U_{mc} = i_c \cdot Z_g$$

$$\text{For } Z_g = 50k\Omega$$

$$\text{and } i_c = 0.2\mu A_{rms}$$

$$U_{mc} = 10mV_{rms}$$

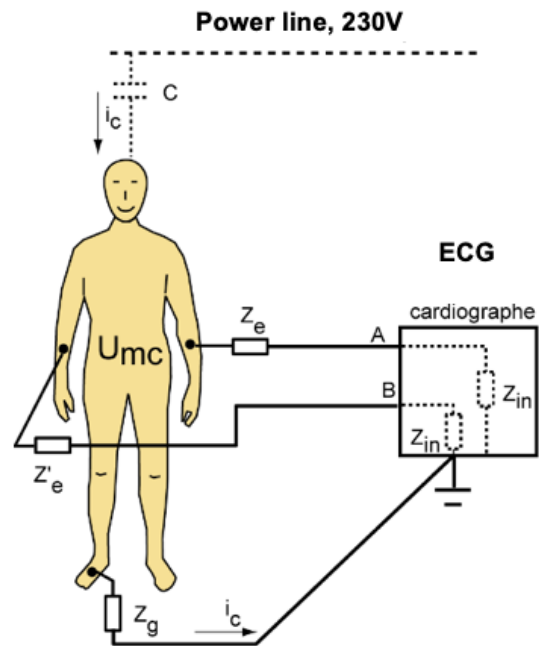Higher in amplitude than
ECG voltage to measure!




$I_c = 0.2 \text{ mA}$?

Model of a differential amplifier

$$\begin{aligned}
 U_o &= A_2 \cdot U_A - A_1 \cdot U_B \\
 &= A_2 \left(U_{mc} + \frac{U_{AB}}{2} \right) - A_1 \left(U_{mc} - \frac{U_{AB}}{2} \right) \\
 &= \underbrace{(A_2 - A_1)}_{A_c} U_{mc} + \underbrace{\frac{A_1 + A_2}{2}}_{A_d} U_{AB}
 \end{aligned}$$

Common mode gain Differential gain

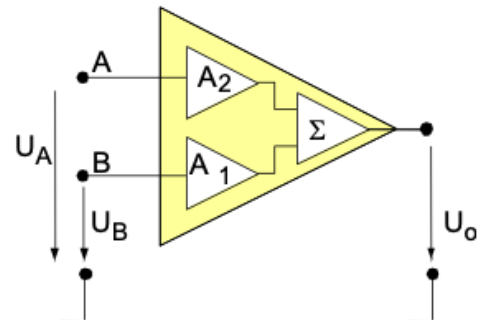

- Differential Gain (A_d)
- Common Mode Rejection Ratio (CMRR)

$$CMRR = \frac{A_d}{A_c} \qquad U_o = A_d \left(U_{AB} + \frac{1}{CMRR} \right) U_{mc}$$


$$CMRR_{dB} = 20 \log_{10} \left| \frac{A_d}{A_c} \right|$$

Model of a differential amplifier

$$U_0 = A_d U_{AB} + A_c U_{mc} \quad CMRR = \frac{A_d}{A_c}$$


$$U_A = U_{mc} + \frac{U_{AB}}{2}$$

$$U_B = U_{mc} - \frac{U_{AB}}{2}$$

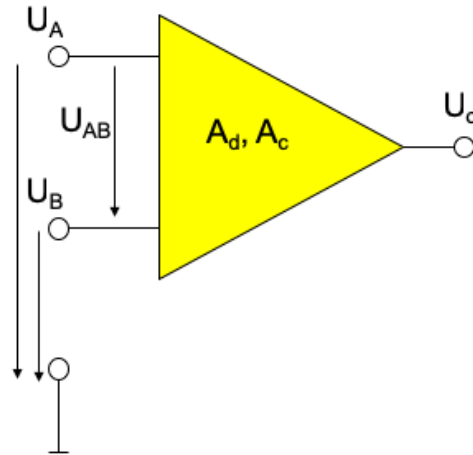

Differential circuit with several stages


Power line, 230V

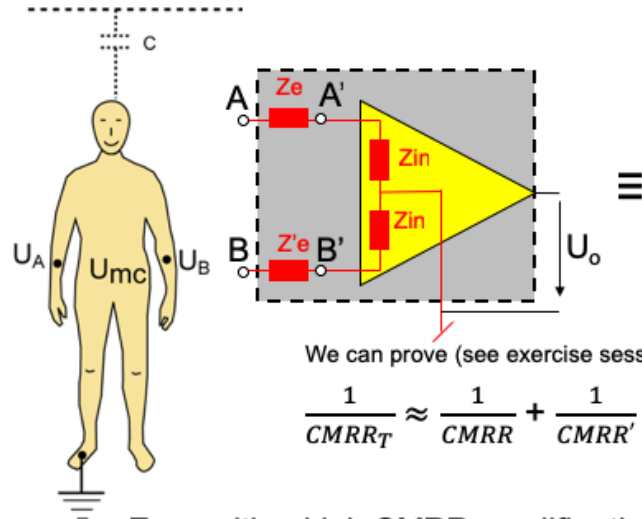

We can prove (see exercise session):

$$\frac{1}{CMRR_T} \approx \frac{1}{CMRR} + \frac{1}{CMRR'}$$

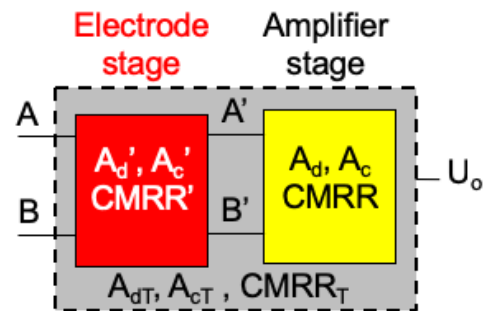Even with a high CMRR amplifier the electrode asymmetry may degrade the performance \rightarrow decrease U_{mc}



III




Remarks

- The skin-electrode contact impedance should be considered in order to reduce the noise of a potential amplifier.
- Decreasing the effect of U_{mc} by minimizing the electrode-skin contact impedance or by increasing the value of Z_{in} and the **CMRR**.

Instrumentation amplifier

- Tunable differential gain from 1 to 10'000, up to 100 Hz (decreasing thereafter with frequency)
- **Input impedance** is very high: $10^{10}\Omega$ in parallel with a few pF
- **Output impedance** is very low (0.1Ω)
- Polarization current at input is very low (few pA to few nA)
- High thermal stability
- High **CMRR** (100 dB and more up to 50 Hz)

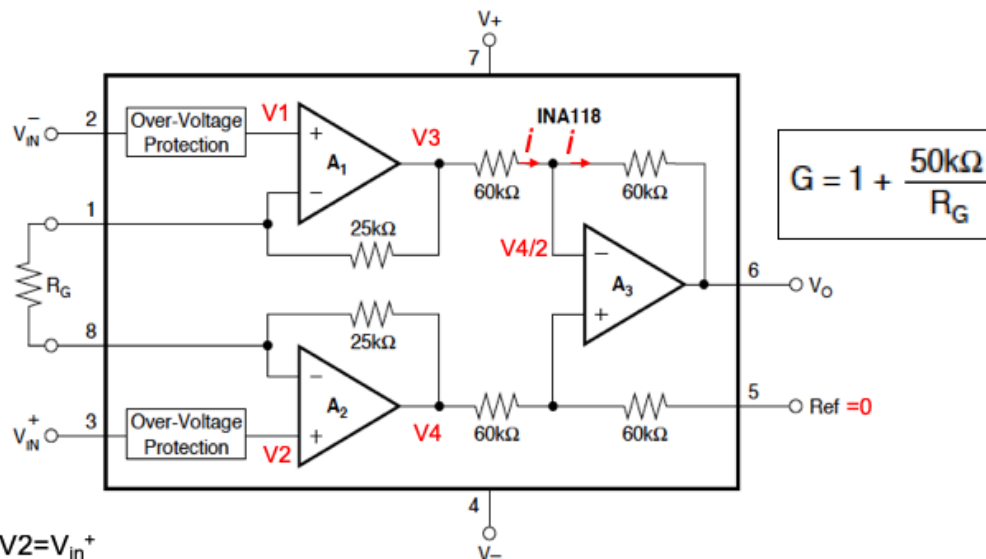Example: INA 118 from Burr-brown CMRR=110dB for $G=1000$ and bandwidth of 7kHz.



$V1=V_{in}^-$, $V2=V_{in}^+$

In the voltage divider: $25k/R_G/25k$: $V2-V1=(R_G/(R_G+50k))(V4-V3) \rightarrow V4-V3=(1+50k/R_G)(V2-V1)$


For amplifier A3: $V3-V4/2=V4/2-V_O \rightarrow V_O=V4-V3=(1+50k/R_G)(V2-V1)=(1+50k/R_G)(V_{in}^+-V_{in}^-)$

$$V_O=(1+50k/R_G)(V_{in}^+-V_{in}^-)$$

Decreasing common mode voltage (1)

The measurement amplifier is wired to the ground
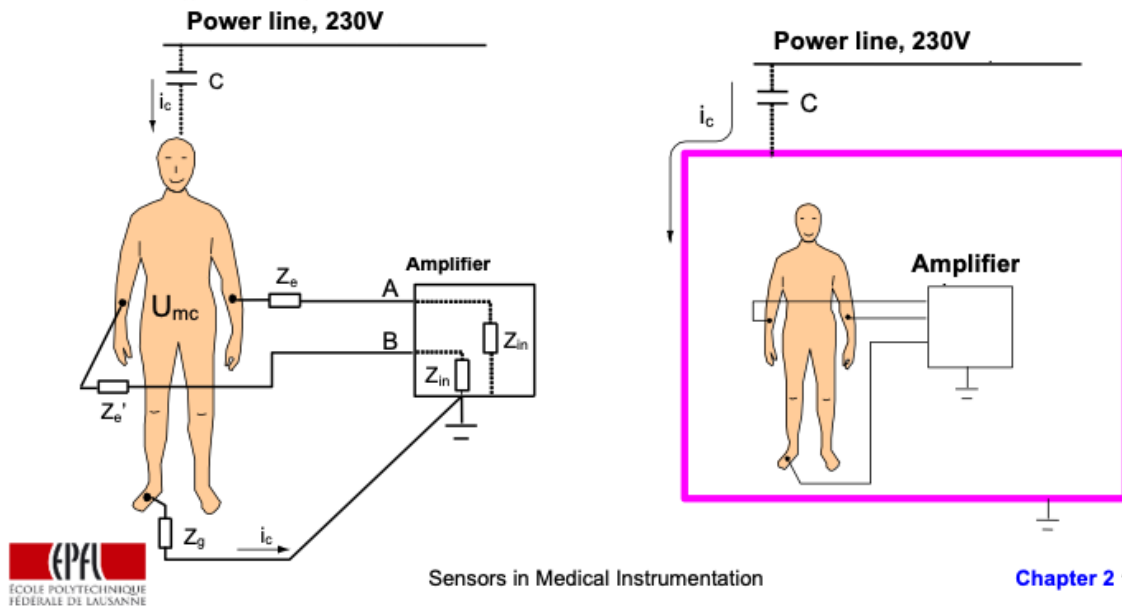
$$U_{mc} = f(i_c) = f(C) \Rightarrow \text{decrease } C \Rightarrow \text{electrostatic shielding}$$




Decreasing common mode voltage (2)

The measurement amplifier is not wired to ground

$$i_c = f(C, C_{a1}, C_{a2}, C_g)$$

⇒ reduce C_{a1} et C_{a2}

⇒ shielding of the amplifier

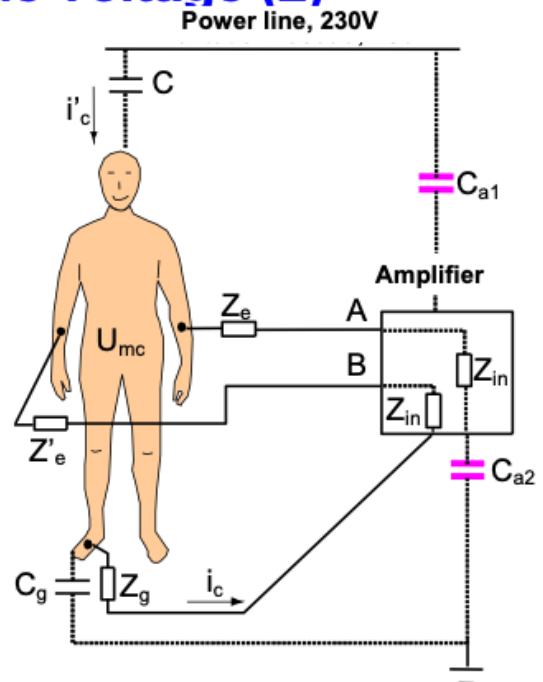

Decreasing common mode voltage (3): "Driven Right Leg": DRL

DRL

Sum of currents in **1**:


$$\frac{2U_{mc}}{R_a} + \frac{U_o}{R_f} = 0$$

$$U_o = -2U_{mc} \frac{R_f}{R_a}$$


in **2**:

$$U_{mc} = R_o i_d + U_o = R_o i_d - 2U_{mc} \frac{R_f}{R_a}$$
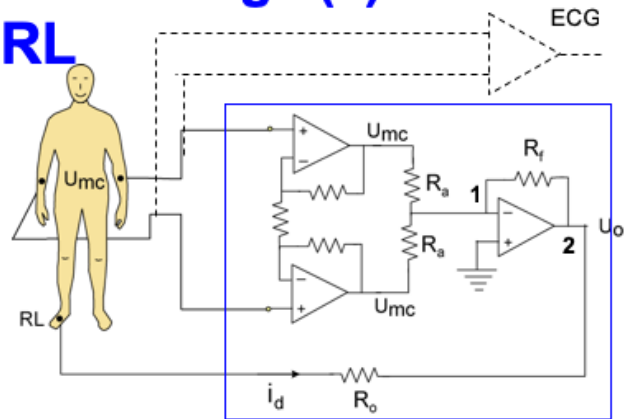
$$U_{mc} = \frac{R_o i_d}{1 + 2 \frac{R_f}{R_a}}$$



Equivalent circuit

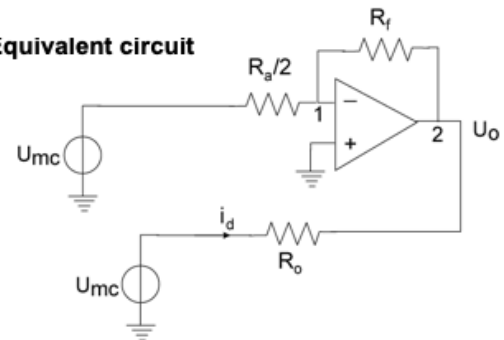

DRL circuit

■
$$U_{mc} = \frac{R_o i_d}{1 + 2 \frac{R_f}{R_a}}$$

For $R_f \gg R_a$, U_{mc} can be considerably decreased.

Ex.: $R_o = 100k$, $R_f = 5M$, $R_a = 25k$, $i_d = 0.2 \mu A_{rms}$

$U_{mc} = 50 \mu V$ (instead of $10 mV$ in the previous case)


Protection against accidental power surge

- If the subject touches a conductor (230V) the output of the amplifier (2) saturates:


$$U_o = U_{sat} = 15V$$

- For $R_o = 5M\Omega$, the current in the subject is:
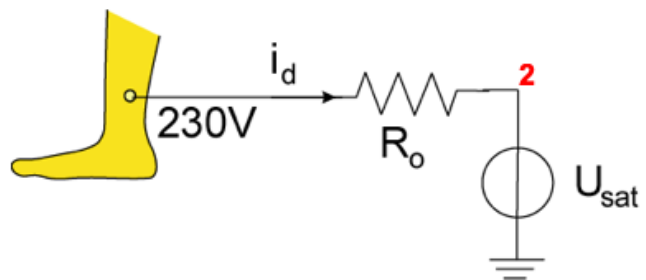
$$i_d = \frac{230 - 15}{5 \cdot 10^6} = 43 \mu A$$





Example: DRL circuit

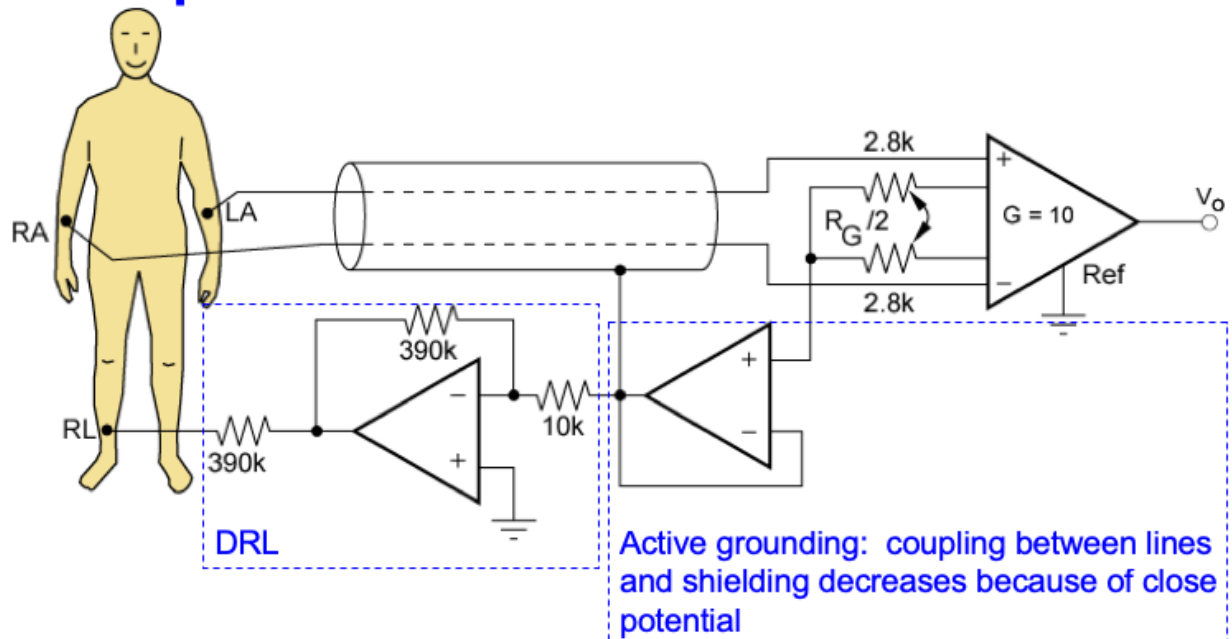

What if only two electrodes are available? (e.g. Defibrillator)

Defibrillator

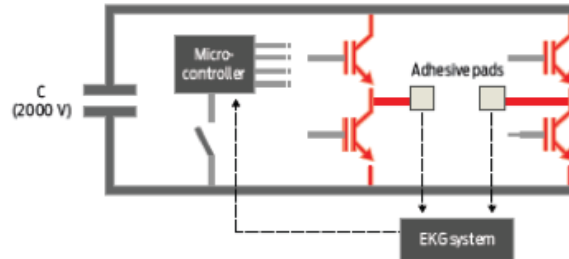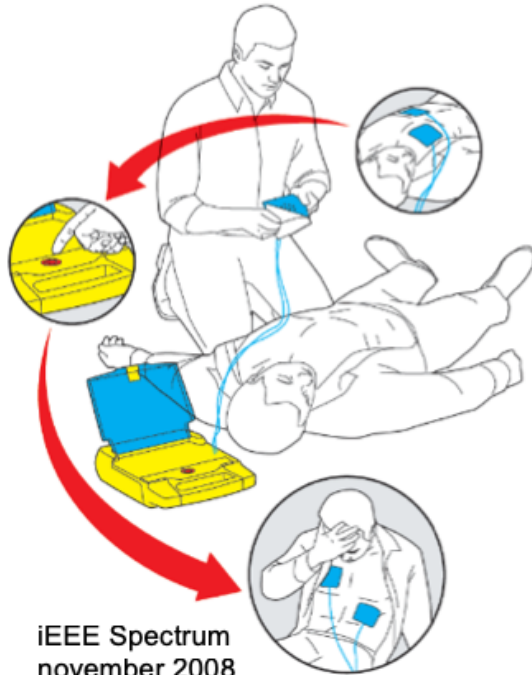

Two electrodes to measure the ECG


Use the average of the two electrode (U_{mc}) as reference

IEEE Spectrum
november 2008




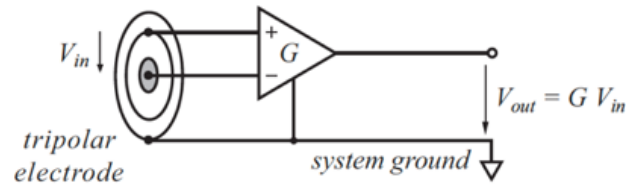Example of reference electrode

- Localised bioelectric signal (EMG, ENG)



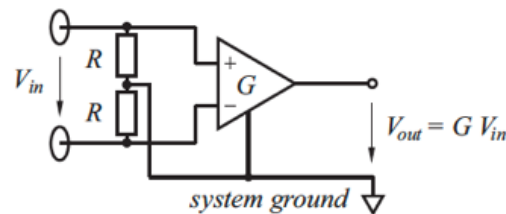- ECG belt with two electrodes
 - Common-mode voltage derived by a voltage divider



T. Werner Degen, ETHZ thesis 19640, 2011



Sensors in Medical Instrumentation

Chapter 2 -46

Tripolar electrodes are used to measure well located differential signals as for example the electrical activity of a nerve at a particular spot

Isolation amplifier

- Decreases common mode voltage U_{mc} that is very high (disconnection in the ground loop)
- Protection of subjects against power surges
 U_{mc2} very high

Stage A_1 : instrumentation amplifier


Stage A_2 : amplifier of gain 1

C_1 : wired to the ground of the source


C_2 : wired to earth or ground

Isolation barrier: total disconnection of ohmic connection

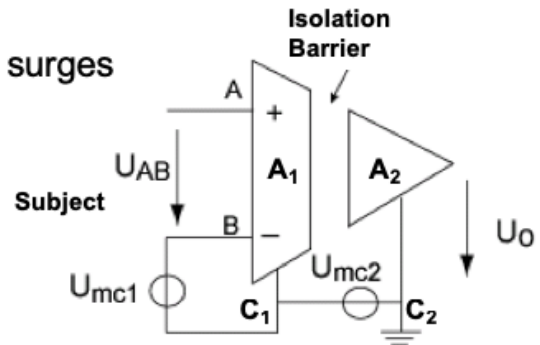Between A_1 et A_2 , transfer of signal by electric coupling (magnetic, optic)





Isolation amplifier

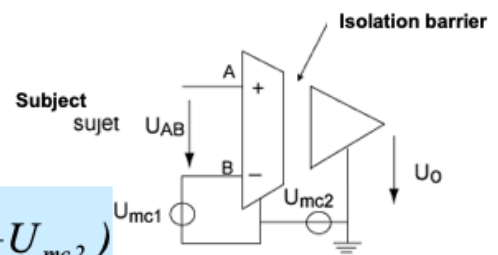


- $$U_o = A_d \left(U_{AB} + \frac{1}{CMRR} U_{mc1} + \frac{1}{IMRR} U_{mc2} \right)$$
- CMRR : common mode rejection ratio (>100dB)
- IMRR : Isolation mode rejection ratio (> 140dB)
- A_d : differential gain
- U_{mc1} : common mode voltage of the subject (tens of volts)
- U_{mc2} : common mode voltage of the device (can reach hundreds of volts)

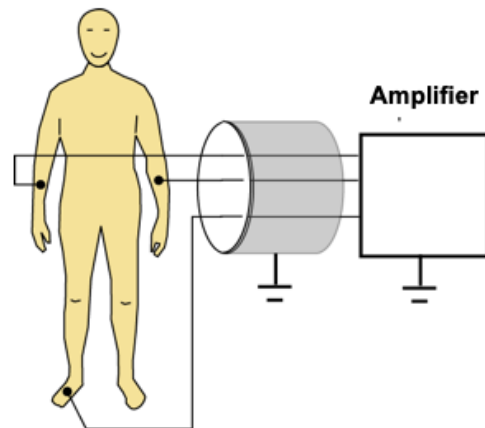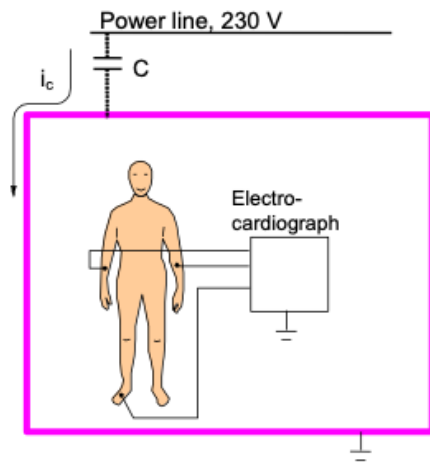Electrostatic shielding and protection against magnetic field




Protection against magnetic field

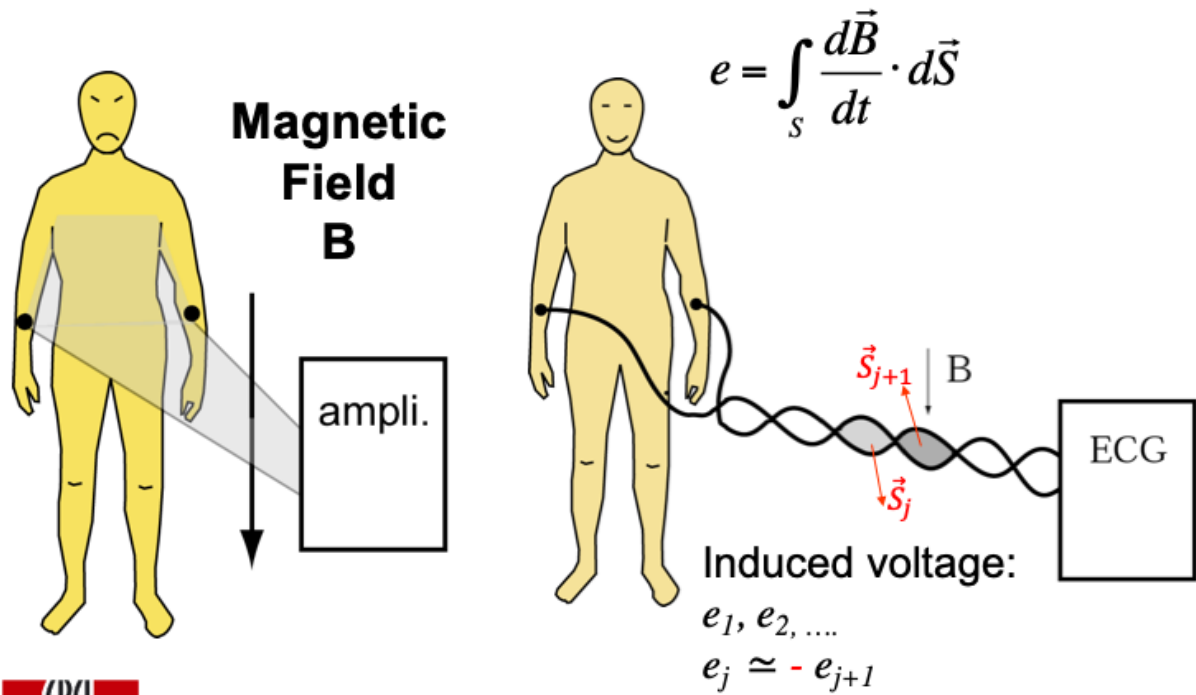


Example

- For $U_A > U_B$, $U_A < U_{mc} < U_B$

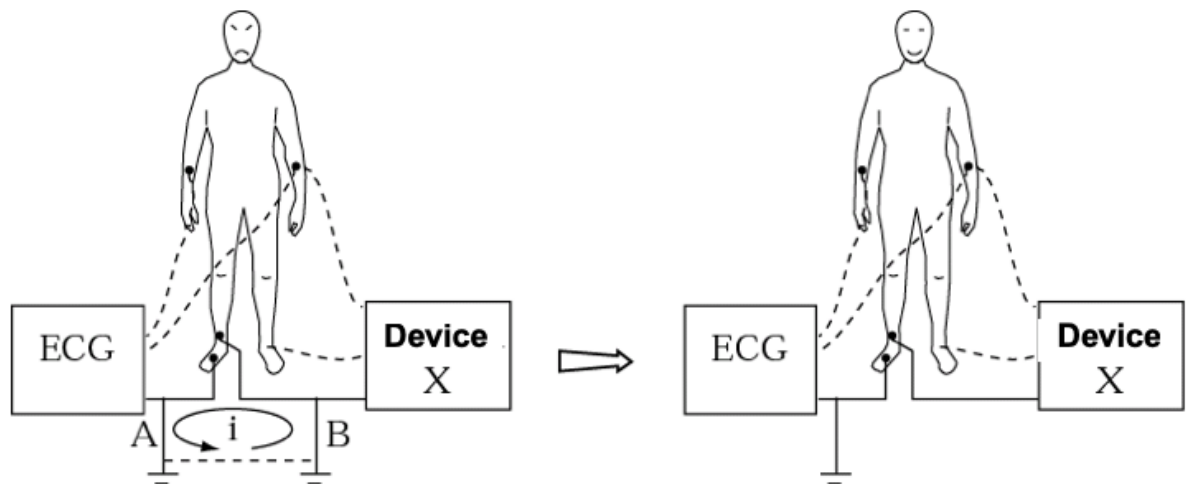


Grounding

- $R_c \ll R$ internal of the amplifier

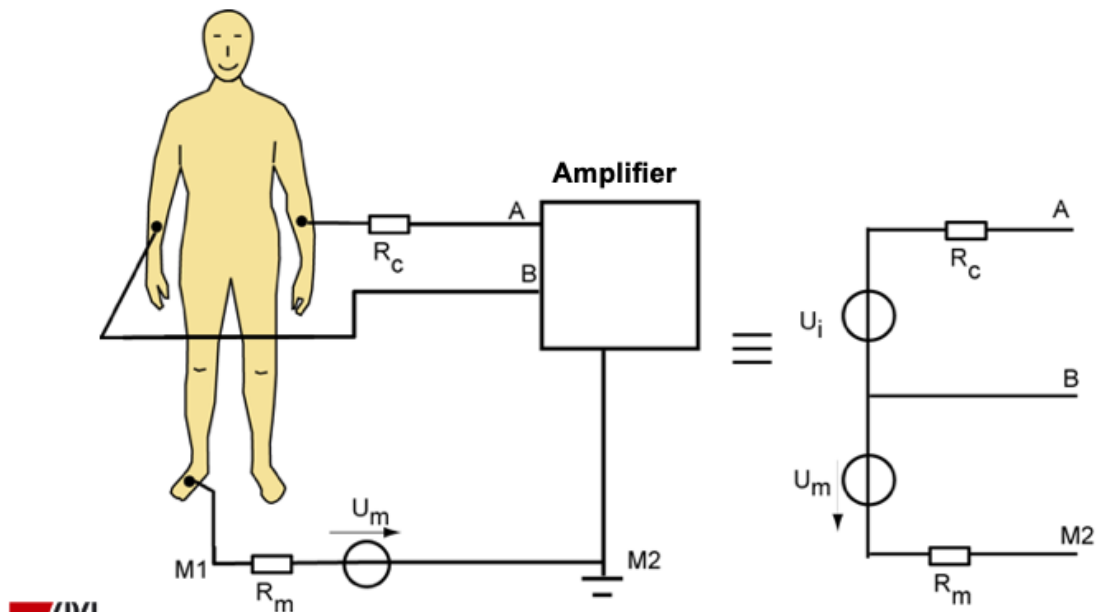


Wiring of asymmetrical amplifiers

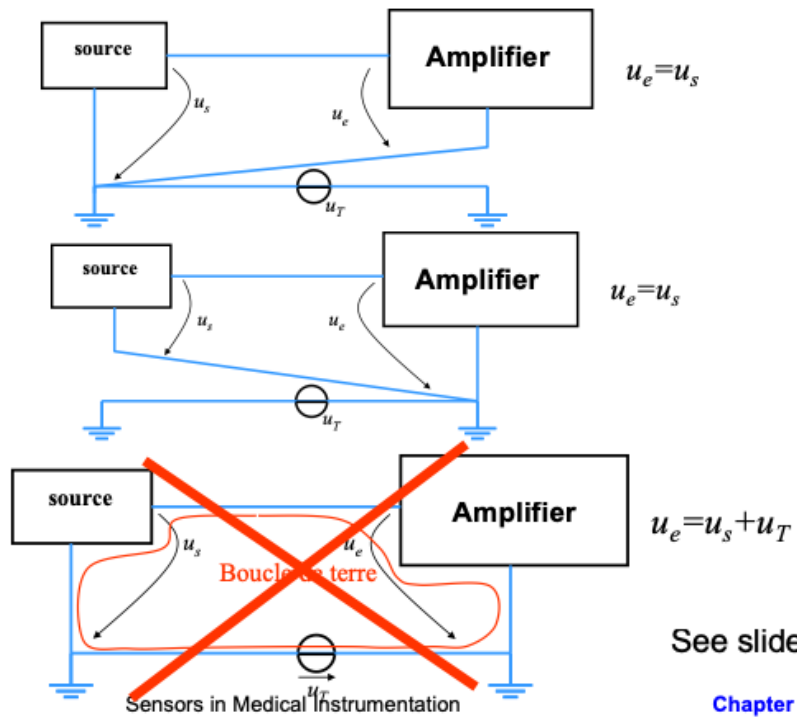

See slide 31

Chapter 2 -53

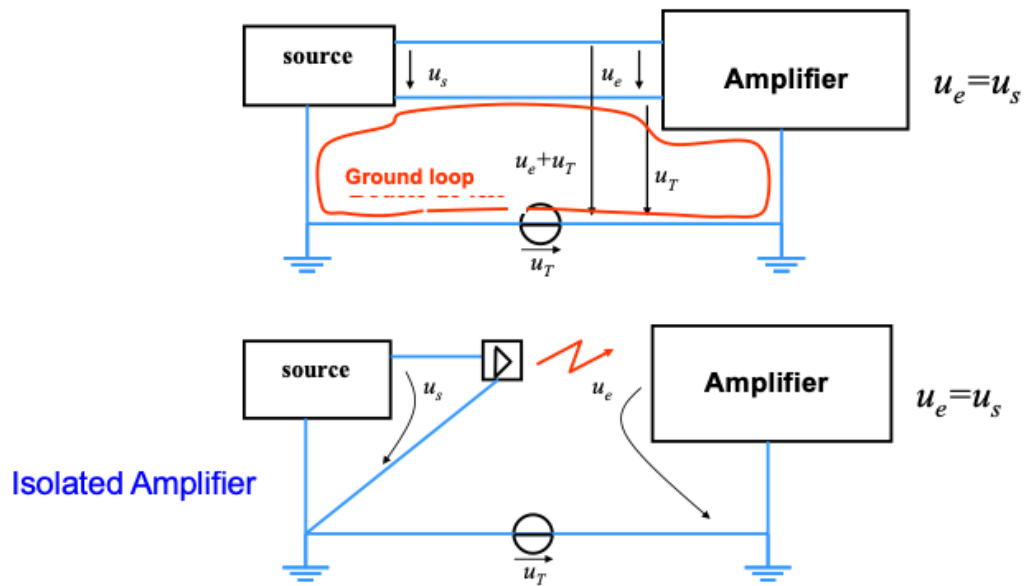Wiring of differential and insulating amplifiers



Electrical filtering

- Low-pass (anti-aliasing, sampling)
- High-pass (offset, drift)

- Non-stationary signals
 - Adaptative filtering
 - Wavelet

Next lecture

- Chapter 3:
Biopotential measurement

Annex: thermal noise model

- Noise power provided at charge:

$$P_{N,L} = R_L I_N^2 = \frac{R_L}{(R_N + R_L)^2} U_{Neff}^2$$

- The **maximum noise power** that this source can provide exteriorly is when $R_N = R_L$,

$$P_N = \frac{1}{4R_N} U_{Neff}^2 = KTB_N$$

$$U_{Neff}^2 = 4KTR_N B_N$$

- The noise from measurement devices (amplifier or voltmeter) is also expressed in V^2/Hz , or V/\sqrt{Hz}